


ELCT 221 Project 2

Transfer Functions


Will Rashley and Carson Murray

## Experiment 1: Low-Pass Filter


Schematic Picture:

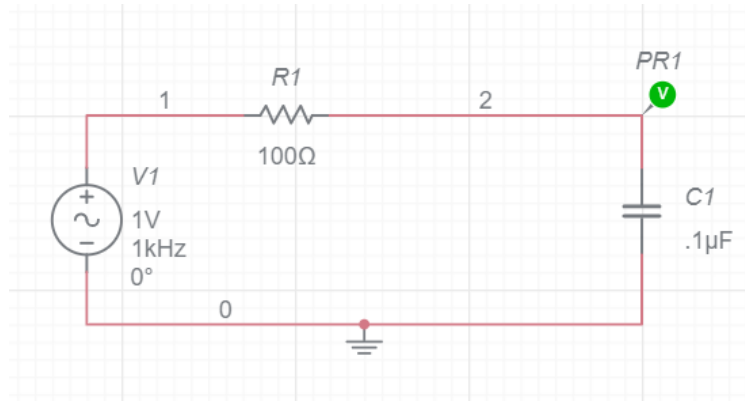


Breadboard Connections:

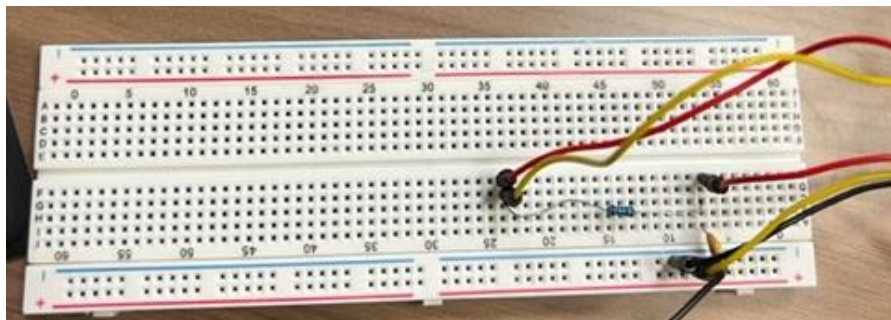

Measured Transfer Functions:

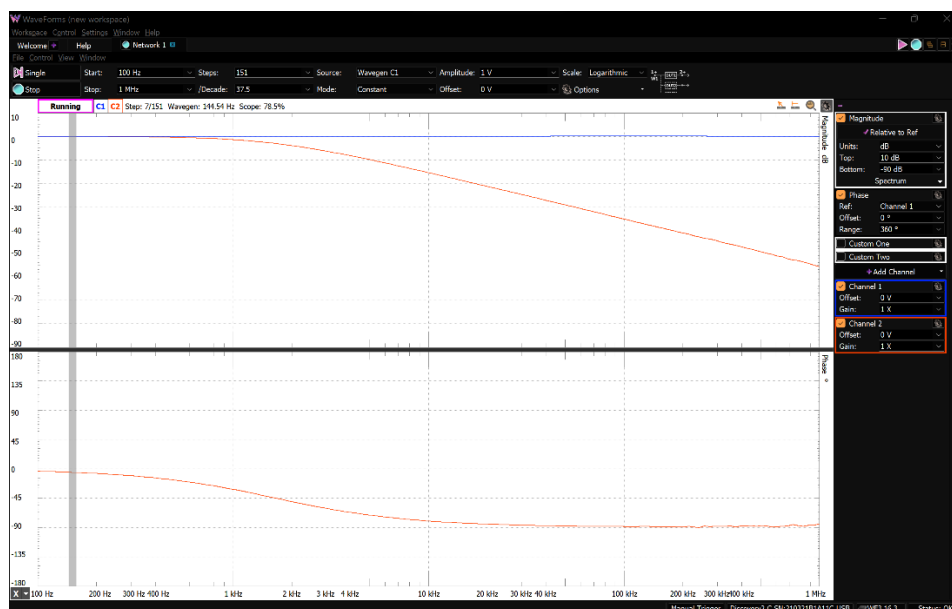

## Spice Simulation Transfer Functions:

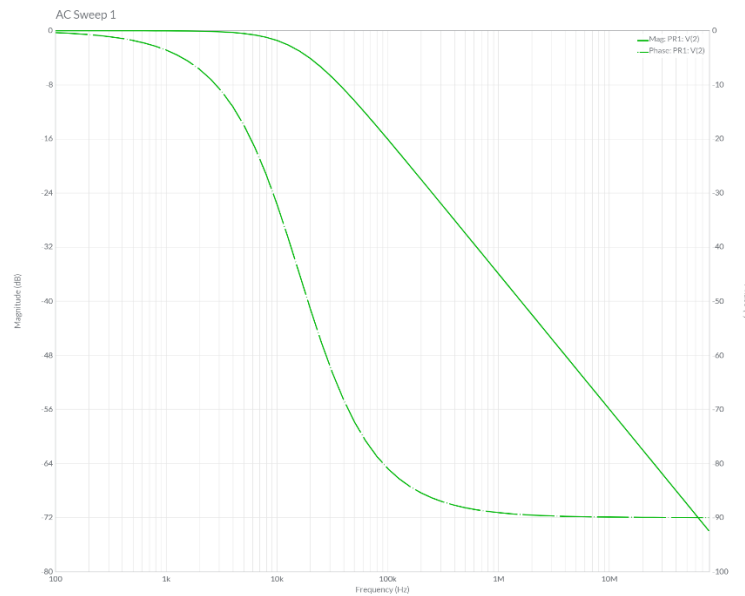

### Estimation of Corner Frequency:


$$\omega_c = \frac{1}{RC} = \frac{1}{100 \, \Omega * 0.1 \, \mu F} = 100 \, kHz$$

### Comments:


The low-pass filter transfer functions for both the simulated and measured graphs were both a success in capturing the correct shape for a low-pass filter. Although, the measured transfer functions appear to be shifted a to the left as they should be closer to the corner frequency of 100 kHz.

## Experiment 2: High-Pass Filter


Schematic Picture:

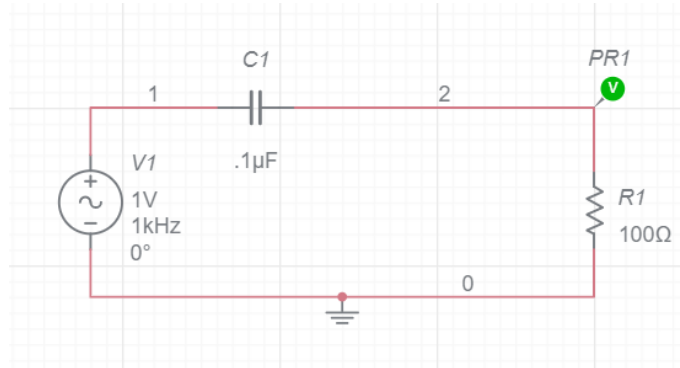


Breadboard Connection:

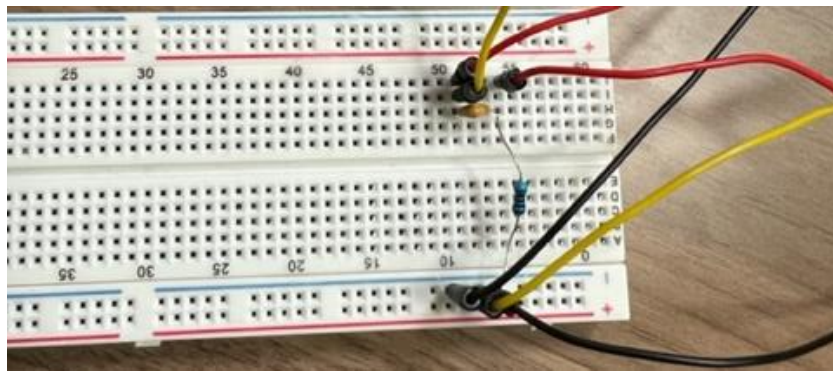

Measured Transfer Functions:

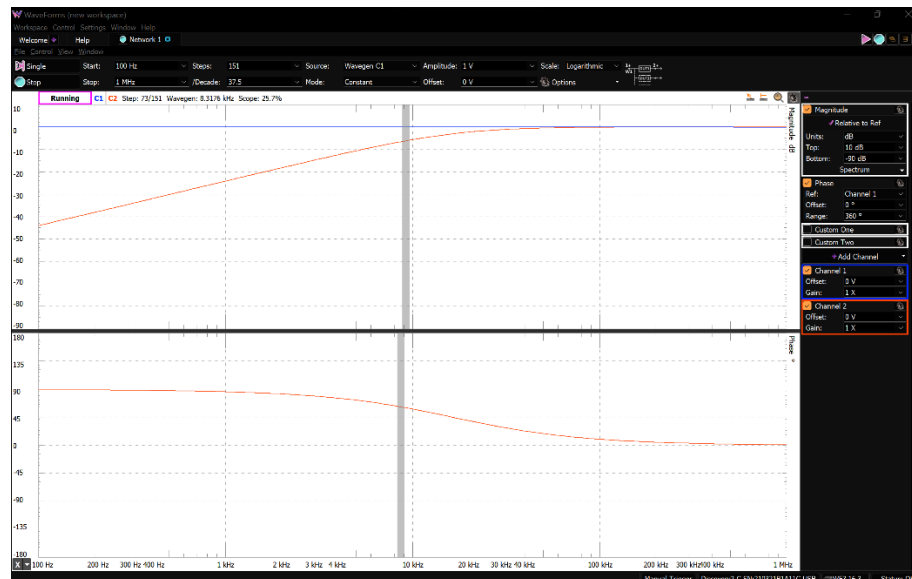

## Spice Simulation Transfer Functions:

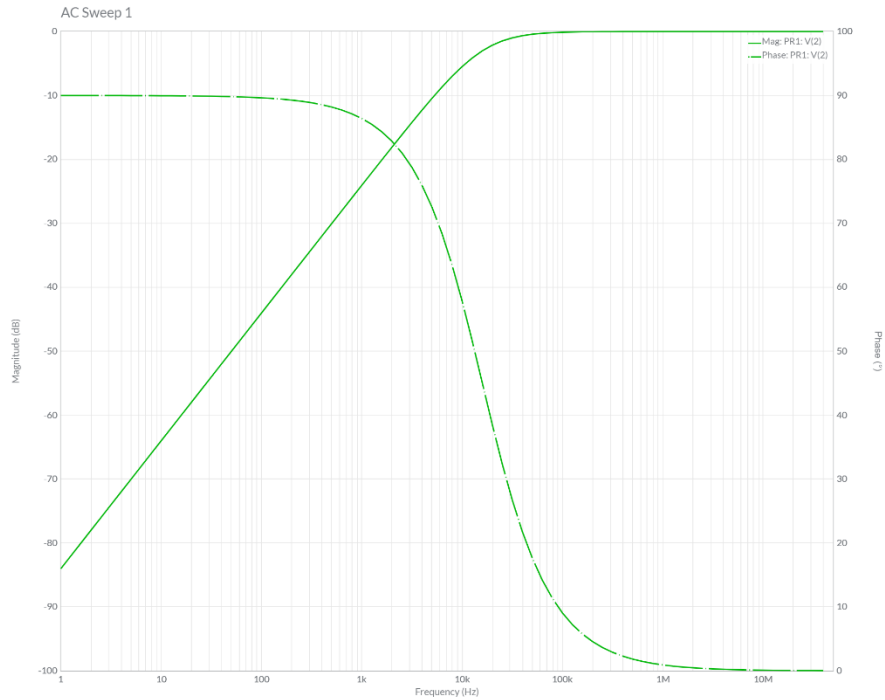

## Estimation of Corner Frequency:


$$\omega_c = \frac{1}{RC} = \frac{1}{100 \, \Omega * 0.1 \, \mu F} = 100 \, kHz$$

## Comments:


The measured high-pass transfer function and simulated high-pass transfer function both appear to capture the correct shape and correct corner frequencies.

## Experiment 3: LC Band-Pass Filter


Schematic Picture:

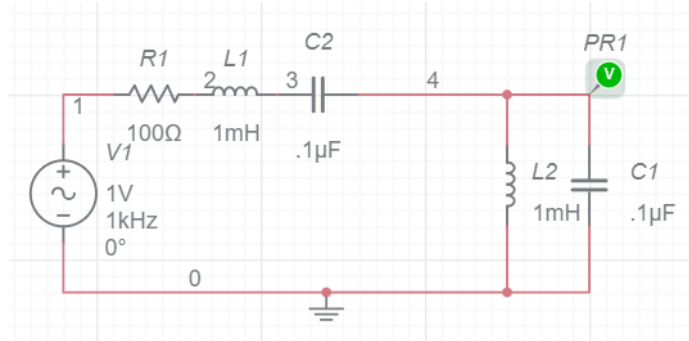


Breadboard Connection:

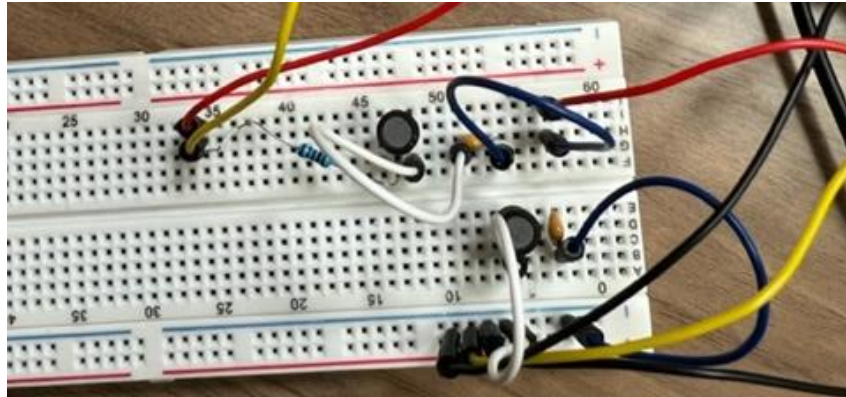

Measured Transfer Functions:

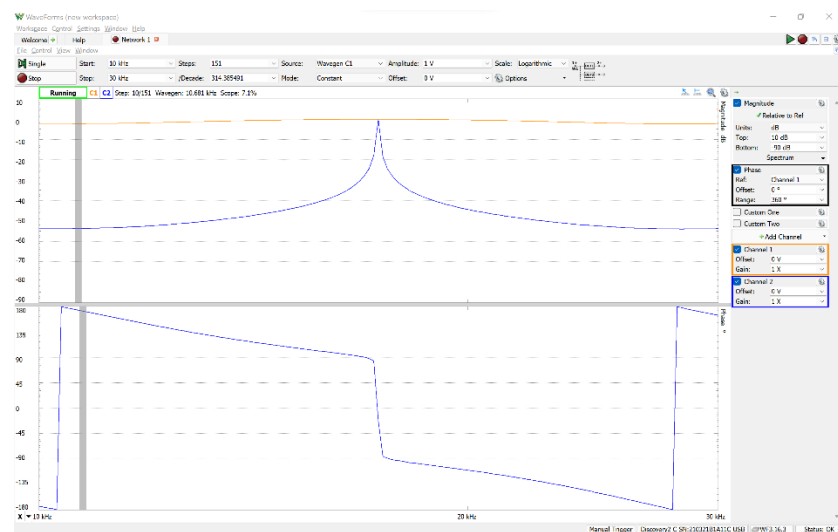

## Spice Simulation Transfer Functions:

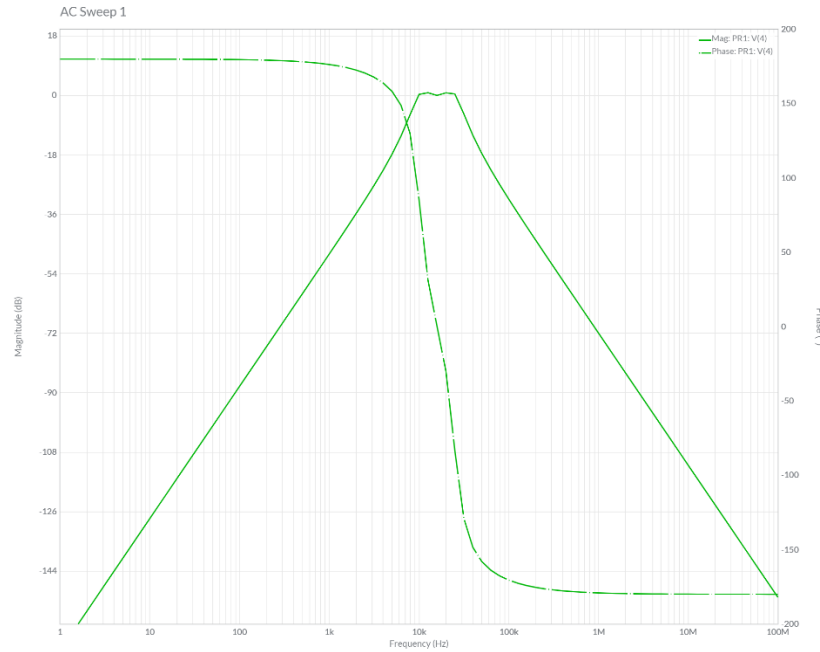

### Estimation of Resonance Frequency:

$$\omega_r = \frac{1}{2 * \pi * \sqrt{L * C}} = \frac{1}{2 * \pi * \sqrt{1 \text{ mH} * 0.1 \mu\text{F}}} \approx 15.9 \text{ kHz}$$

### Comments:

Both Simulated and measured graphs appear to be very similar in shape and scale. The only differences being that the measured amplitude appears to only touch 0 once (unlike the simulated which stays at zero for a couple thousand Hz) and the phase graph appears to be slightly wild towards the beginning and end of the graph.